
## Homework02


1.

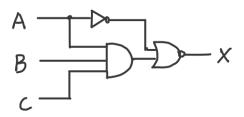



Α _	
	47 - v
в —	
c –	


a	b	c	x	_ <b>y</b> _
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

2.

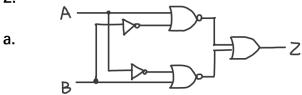

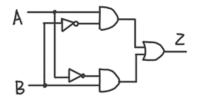


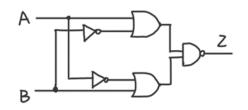

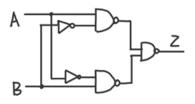


除了以上画法外,每个 — 一 都可以替换成 — 或 一 或 一 立 一 在这种情况下,所需的最少 MOS 晶体管数为 16 个,为上面给出的最后一个图。

b.

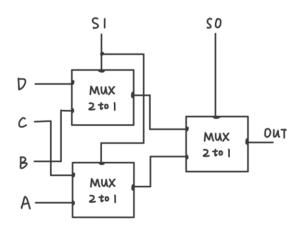

{s1,s0}	选择的信号
00	А
01	В
10	С
11	D

3.

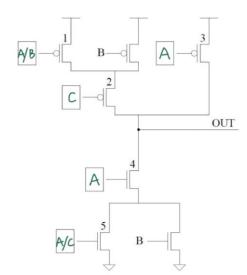


	A	В	C	OUT
	0	0	0	1
Ī	0	0	1	1
	0	1	0	1
I	0	1	1	1
	1	0	0	1
	1	0	1	0
	1	1	0	0
	1	1	1	0


4. 对图 3.36, A 从 0 变为 1 时 D 的输出从 C 变为 B。

对图 3.37, A从 0 变为 1 时 D 的输出从 1 变为 B

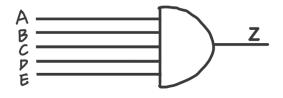
- 5. a. 3 个门延迟
  - b. 12 个门延迟
  - c. 如图, 延迟减少为1个门延迟



6.

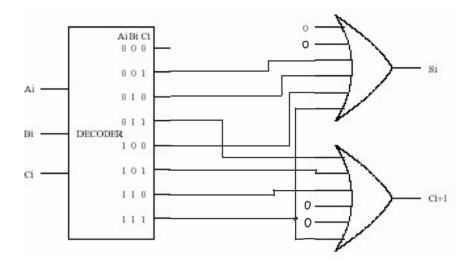

7.

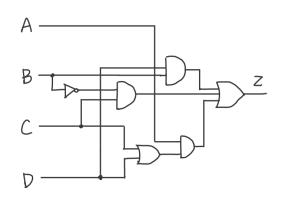


$\overline{}$				
A	В		D	Z
*	*	0	0	0
0	0	0	ı	0
0	0	1	0	1
0	0	1	ı	I
0	ı	0	-	1
0	ι	1	0	0
0	١	1	l	1
1	0	0	J	J
l	ט	- 1	0	1
ı	0	I	l	١
J	ı	0	١	١
١	ı	1	0	1
1	Ī	1	l.	l

8.


*Ο*\.

Α	В	G	E	L
0	0	0	1	0
0	1	0	0	1
ı	0	1	0	0
1	ι	0	1	Ð

b.

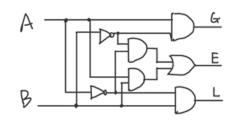

C.

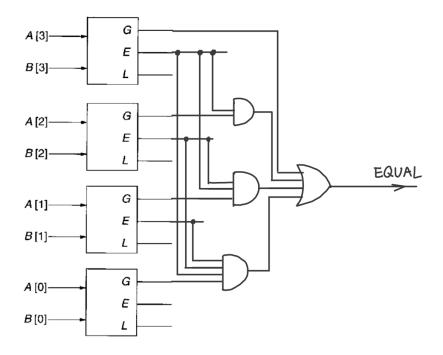

- 9.50个时钟周期后,前两个 D 锁存器输出为 1,后四个输出为 0 6 个时钟周期
- 10.
- a. 一共存在 100\*100\*4\*100\*4\*101\*2\*16\*60=3102720000000 介于 2<sup>41</sup>与 2<sup>42</sup>之间,共需要 42bit 进行储存
- b. 一共需要 2\*7+2+7+2+7+1+4+6=43bit 进行存储
- **c.** b 只比 a 多需要一位储存空间,但在可读性以及数据输出时需要的计算量上节 省了大量的时间

11. a.

a	Ь	X
00	00	00
00	0	<i>90</i>
00	10	10
00	1/	11
01	00	01
01	01	01
01	10	0]
01	11	١١
10	00	00
10	01	10
10	10	10
10	11	10
1.1	00	00
11	01	01
1.1	10	11
1.1	11	1.1

其中a.b.×均为 ZbH住崑

- a 表示当前楼层
- 占表示清求前往楼层
- x 表示清求之后电梯停留的楼层

